


EEE 2015 ELECTRICS


L03 AC Circuit Analysis & Power Calculations

Behaviors of Basic Circuit Components under AC

Resistor (R)


Resistor 100 Ω

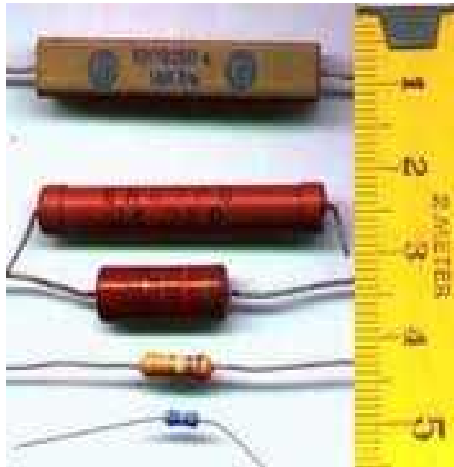 $R = 100 \Omega$
 $X = 0 \Omega$
 $Z = 100 \Omega \angle 0^\circ$



Coil (L) (Inductor)


Inductor 100 mH
159.15 Hz

 $R = 0 \Omega$
 $X = 100 \Omega$
 $Z = 100 \Omega \angle 90^\circ$



Capacitor(C) (Condenser)

Capacitor 10 μF
159.15 Hz

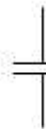 $R = 0 \Omega$
 $X = 100 \Omega$
 $Z = 100 \Omega \angle -90^\circ$



AC circuit –RL in series

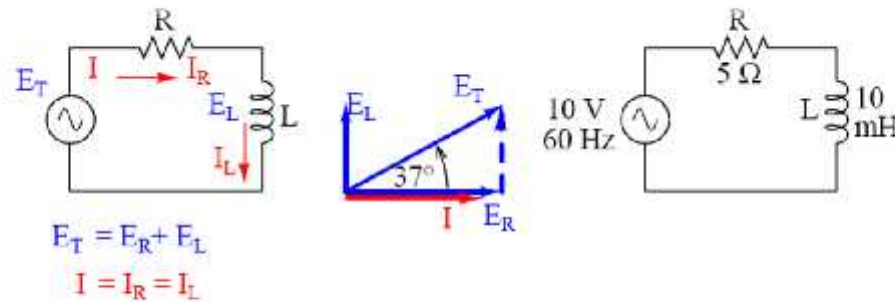


Figure 3.10: Series resistor inductor circuit: Current lags applied voltage by 0° to 90° .

Inductive reactance of the coil

$$X_L = 0 + 3.7699j\Omega$$

The total effect is called as **impedance**.

$$Z = R + X_L = 5 + 3.7699j\Omega = 6.262 \angle 37.016^\circ \Omega$$

$$Z = \frac{V}{I}$$

$$I = \frac{10 \angle 0^\circ \text{ V}}{6.262 \angle 37.016^\circ \Omega} = 1.597 \angle -37.016^\circ \text{ A}$$

AC circuit –RL in series

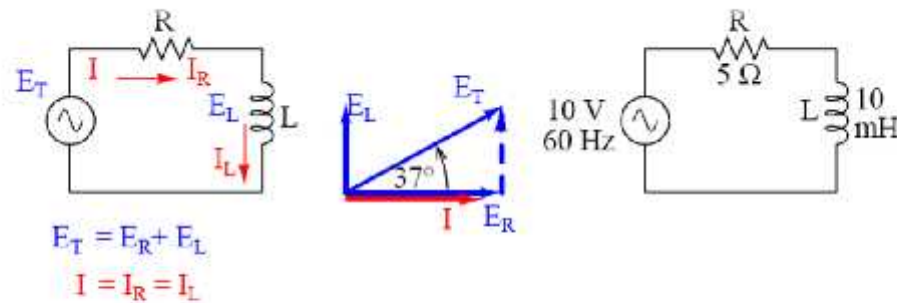
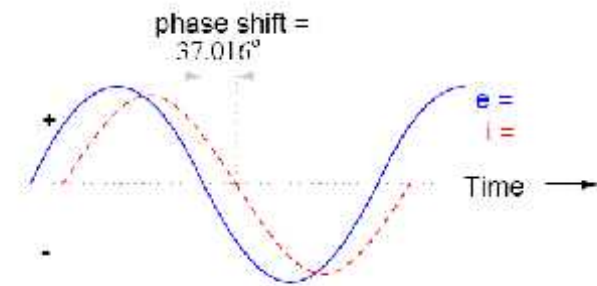
Figure 3.10: Series resistor inductor circuit: Current lags applied voltage by 0° to 90° .

Figure 3.11: Current lags voltage in a series L-R circuit.

$$E = IZ$$

$$E = IZ$$

$$E_R = I_R Z_R$$

$$E_L = I_L Z_L$$

$$E_R = (1.597 \text{ A} \angle -37.016^\circ)(5 \Omega \angle 0^\circ)$$

$$E_L = (1.597 \text{ A} \angle -37.016^\circ)(3.7699 \Omega \angle 90^\circ)$$

$$E_R = 7.9847 \text{ V} \angle -37.016^\circ$$

$$E_L = 6.0203 \text{ V} \angle 52.984^\circ$$

Notice that the phase angle of E_L is exactly 90° more than the phase angle of the current.

$$E_{\text{total}} = E_R + E_L$$

$$E_{\text{total}} = (7.9847 \text{ V} \angle -37.016^\circ) + (6.0203 \text{ V} \angle 52.984^\circ)$$

$$E_{\text{total}} = 10 \text{ V} \angle 0^\circ$$

AC circuit –RL in parallel

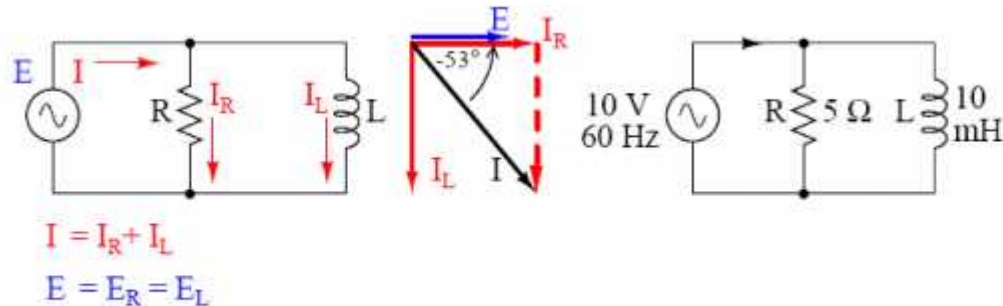


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I				Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 + j3.7699$ $3.7699 \angle 90^\circ$		Ohms

Rule of parallel circuits:

$$E_{\text{total}} = E_R = E_L$$

AC circuit –RL in parallel

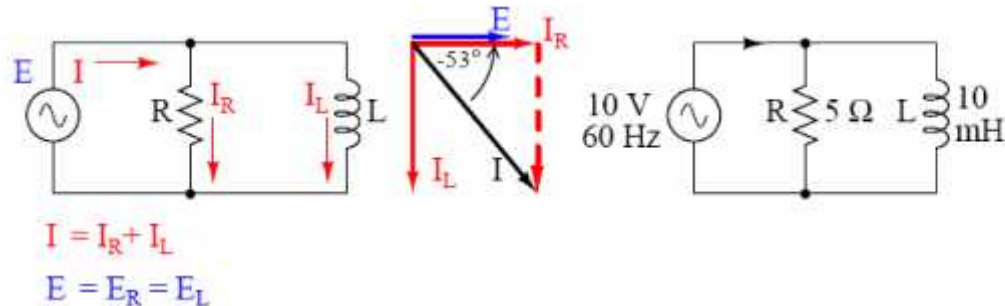


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 - j2.6526$ $2.6526 \angle -90^\circ$		Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 + j3.7699$ $3.7699 \angle 90^\circ$		Ohms

↑

Ohm's Law

$I = \frac{E}{Z}$

↑

Ohm's Law

$I = \frac{E}{Z}$

AC circuit –RL in parallel

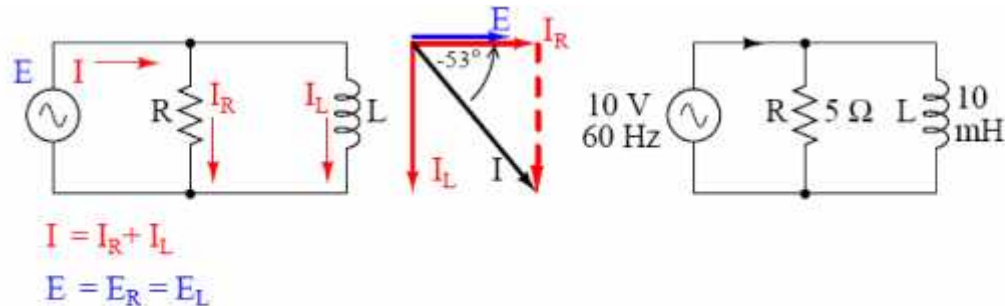


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 - j2.6526$ $2.6526 \angle -90^\circ$	$2 - j2.6526$ $3.3221 \angle -52.984^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 + j3.7699$ $3.7699 \angle 90^\circ$		Ohms

Rule of parallel circuits:

$$I_{\text{total}} = I_R + I_L$$

AC circuit –RL in parallel

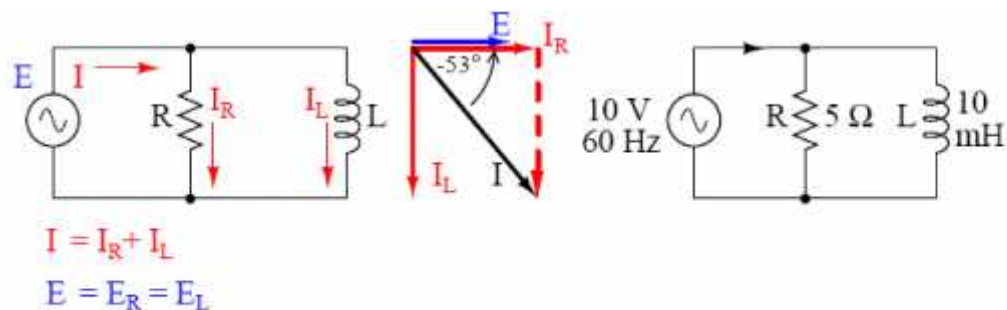


Figure 3.14: Parallel R-L circuit.


	R	L	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 - j2.6526$ $2.6526 \angle -90^\circ$	$2 - j2.6526$ $3.322 \angle -52.984^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 + j3.7699$ $3.7699 \angle 90^\circ$	$1.8122 + j2.4035$ $3.0102 \angle 52.984^\circ$	Ohms

\uparrow
 Ohm's Law or Rule of parallel circuits:

$$Z = \frac{E}{I}$$

$$Z_{\text{total}} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L}}$$

AC circuit –RC in series

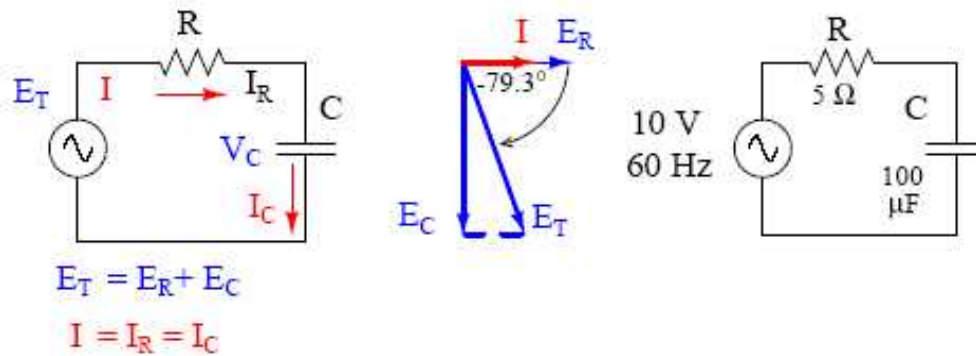

$$X_c = 0 - 26.5258j\Omega$$

$$R = 5 + 0j\Omega$$

$$Z = R + X_c = 5 - 26.5258j\Omega = 26.993 \angle -79.325$$

$$I = \frac{E}{Z}$$

$$I = \frac{10 \text{ V} \angle 0^\circ}{26.933 \Omega \angle -79.325^\circ}$$

$$I = 370.5 \text{ mA} \angle 79.325^\circ$$


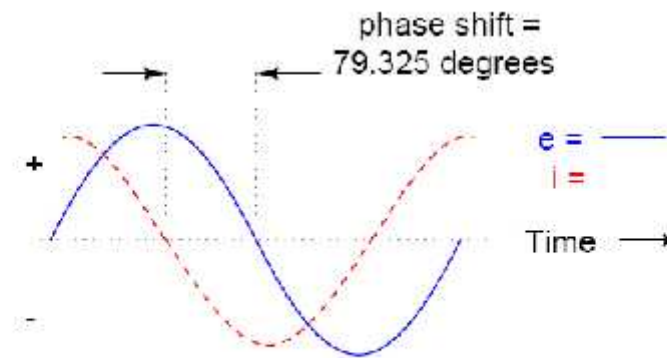


Figure 4.11: Voltage lags current (current leads voltage) in a series R-C circuit.

AC circuit –RC in series

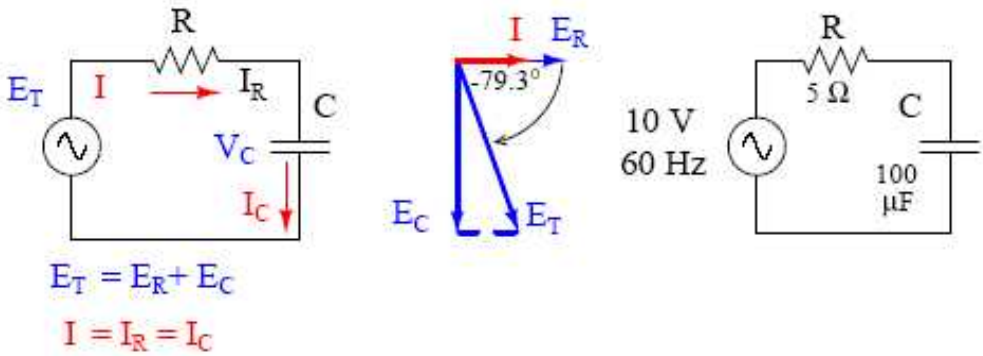


	R	C	Total	
E			$10 + j0$ $10 \angle 0^\circ$	Volts
I			$68.623\text{m} + j364.06\text{m}$ $370.5\text{m} \angle 79.325^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$	$5 - j26.5258$ $26.993 \angle -79.325^\circ$	Ohms

	R	C	Total	
E			$10 + j0$ $10 \angle 0^\circ$	Volts
I	$68.623\text{m} + j364.06\text{m}$ $370.5\text{m} \angle 79.325^\circ$	$68.623\text{m} + j364.06\text{m}$ $370.5\text{m} \angle 79.325^\circ$	$68.623\text{m} + j364.06\text{m}$ $370.5\text{m} \angle 79.325^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$	$5 - j26.5258$ $26.993 \angle -79.325^\circ$	Ohms

Rule of series circuits:

$$I_{\text{total}} = I_R = I_C$$

AC circuit –RC in series

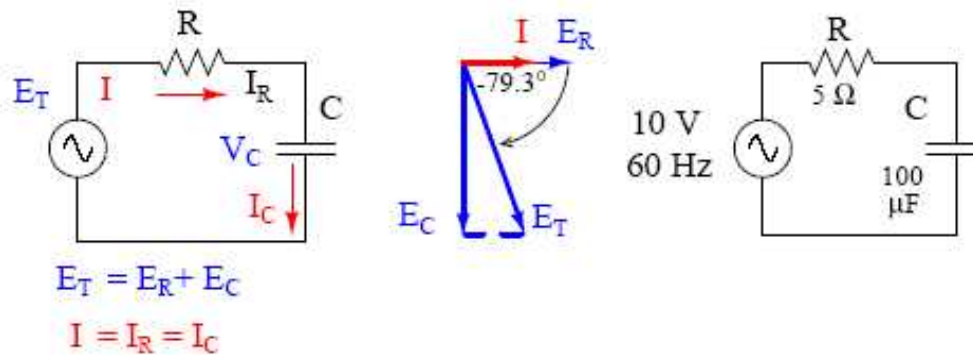

	R	C	Total	
E	$343.11\text{m} + \text{j}1.8203$	$9.6569 - \text{j}1.8203$	$10 - \text{j}0$	Volts
	$1.8523 \angle 79.325^\circ$	$9.8269 \angle -10.675^\circ$	$10 \angle 0^\circ$	
I	$68.623\text{m} + \text{j}364.06\text{m}$	$68.623\text{m} + \text{j}364.06\text{m}$	$68.623\text{m} + \text{j}364.06\text{m}$	Amps
	$370.5\text{m} \angle 79.325^\circ$	$370.5\text{m} \angle 79.325^\circ$	$370.5\text{m} \angle 79.325^\circ$	
Z	$5 + \text{j}0$	$0 - \text{j}26.5258$	$5 - \text{j}26.5258$	Ohms
	$5 \angle 0^\circ$	$26.5258 \angle -90^\circ$	$26.993 \angle -79.325^\circ$	

\uparrow
 Ohm's
 Law
 $V = IZ$


\uparrow
 Ohm's
 Law
 $V = IZ$

As it can be considered easily, the phase shift is 79.325 degrees in this circuit whereas in the circuit that has only one capacitor it was 90 degrees.

The current and the voltage on the resistor is on the same phase as it is mentioned.

However, the current on a capacitor leads voltage by 90 degrees.

AC circuit –RC in parallel

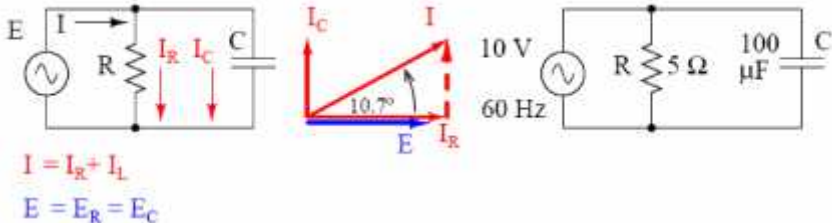


	R	C	Total	
E			$10 + j0$ $10 \angle 0^\circ$	Volts
I				Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$		Ohms

	R	C	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I				Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$		Ohms

Rule of parallel circuits:
 $E_{total} = E_R = E_C$

AC circuit –RC in parallel

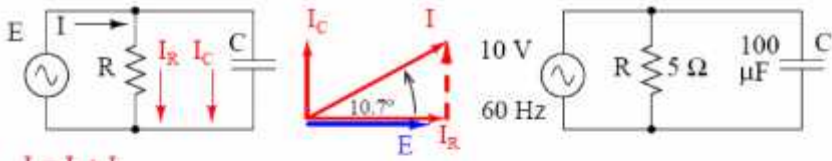

$I = I_R + I_C$
 $E = E_R = E_C$

Figur

	R	C	Total	
E	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	Volts
I	2 + j0 2 ∠ 0°	0 + j376.99m 376.99m ∠ 90°		Amps
Z	5 + j0 5 ∠ 0°	0 - j26.5258 26.5258 ∠ -90°		Ohms

↑
Ohm's Law

$$I = \frac{E}{Z}$$

↑
Ohm's Law

$$I = \frac{E}{Z}$$

	R	C	Total	
E	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	Volts
I	2 + j0 2 ∠ 0°	0 + j376.99m 376.99m ∠ 90°	2 + j376.99m 2.0352 ∠ 10.675°	Amps
Z	5 + j0 5 ∠ 0°	0 - j26.5258 26.5258 ∠ -90°		Ohms

Rule of parallel circuits:

$$I_{total} = I_R + I_C$$

AC circuit –RC in parallel

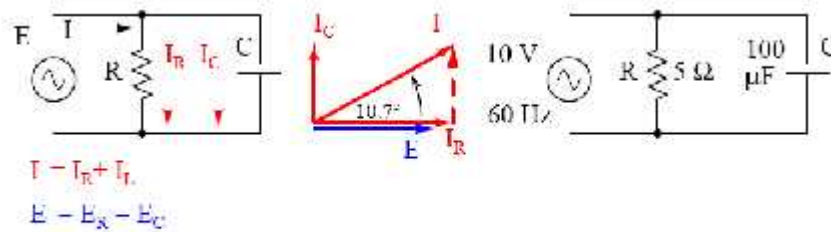


Figure 4.14: Parallel R-C circuit.

	R	C	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 + j376.99\text{m}$ $376.99\text{m} \angle 90^\circ$	$2 + j376.99\text{m}$ $2.0352 \angle 10.675^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$	$4.8284 - j910.14\text{m}$ $4.9135 \angle -10.675^\circ$	Ohms

↑
or


Ohm's Law

$$Z = \frac{E}{I}$$

Rule of parallel circuits:

$$Z_{\text{total}} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_C}}$$

AC circuit –RLC in series

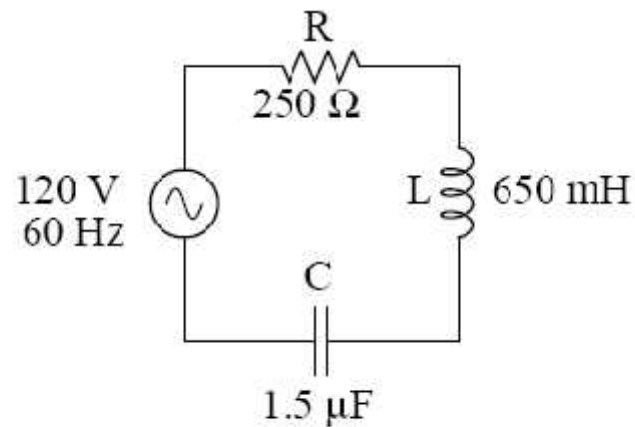Figure 5.2: Example series R , L , and C circuit.

$$X_L = 2\pi fL$$

$$X_L = (2)(\pi)(60 \text{ Hz})(650 \text{ mH})$$

$$X_L = 245.04 \Omega$$

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{(2)(\pi)(60 \text{ Hz})(1.5 \mu\text{F})}$$

$$X_C = 1.7684 \text{ k}\Omega$$

$$Z_R = 250 + j0 \Omega \quad \text{or} \quad 250 \Omega \angle 0^\circ$$

$$Z_L = 0 + j245.04 \Omega \quad \text{or} \quad 245.04 \Omega \angle 90^\circ$$

$$Z_C = 0 - j1.7684 \text{ k}\Omega \quad \text{or} \quad 1.7684 \text{ k}\Omega \angle -90^\circ$$

AC circuit –RLC in series

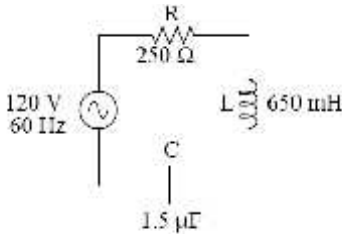


Figure 5.2: Example series R, L, and C circuit.

	R	L	C	Total	
E				120 + j0 120 ∠ 0°	Volts
I					Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°		Ohms

	R	L	C	Total	
E				120 + j0 120 ∠ 0°	Volts
I					Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°	250 - j1.5233k 1.5437k ∠ -80.680°	Ohms

Rule of series circuits:

$$Z_{\text{total}} = Z_R + Z_L + Z_C$$

	R	L	C	Total	
E				120 + j0 120 ∠ 0°	Volts
I				12.589m + j6.708m 77.734m / 80.680°	Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°	250 - j1.5233k 1.5437k ∠ -80.680°	Ohms

Ohm's Law

$$I = \frac{E}{Z}$$

AC circuit –RLC in series

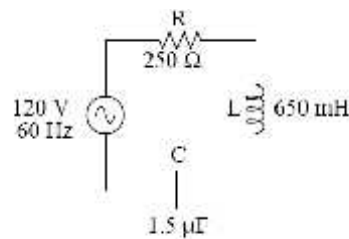


Figure 5.2: Example series R, L, and C circuit.

	R	L	C	Total	
E				120 + j0 120 ∠ 0°	Volts
I	12.589m + j6.708m 77.734m ∠ 80.680°	12.589m + j6.708m 77.734m ∠ 80.680°	12.589m + j6.708m 77.734m ∠ 80.680°	12.589m + j6.708m 77.734m ∠ 80.680°	Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°	250 - j1.5233k 1.5437k ∠ -80.680°	Ohms

Rule of series circuits:
 $I_{\text{total}} = I_R = I_L = I_C$

$E_R + E_L + E_C$ should equal E_{total}

$$\begin{array}{rcl}
 3.1472 + j19.177 \text{ V} & E_R & \\
 -18.797 + j3.0848 \text{ V} & E_L & \\
 135.65 - j22.262 \text{ V} & E_C & \\
 \hline
 120 - j0 \text{ V} & E_{\text{total}} &
 \end{array}$$

	R	L	C	Total	
E	3.1472 + j19.177 19.434 ∠ 80.680°	-18.797 + j3.0848 19.048 ∠ 170.68°	135.65 - j22.262 137.46 ∠ -9.3199°	120 + j0 120 ∠ 0°	Volts
I	12.589m + j6.708m 77.734m ∠ 80.680°	12.589m + j6.708m 77.734m ∠ 80.680°	12.589m + j6.708m 77.734m ∠ 80.680°	12.589m + j6.708m 77.734m ∠ 80.680°	Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°	250 - j1.5233k 1.5437k ∠ -80.680°	Ohms

↑
Ohm's Law
 $E = IZ$

↑
Ohm's Law
 $E = IZ$

↑
Ohm's Law
 $E = IZ$

It should be considered that the amplitude of the voltage on the capacitor is greater than the voltage supplied to the circuit. The influence of the impedance in the whole circuit is smaller than the influence of impedance of any single component. This case causes higher voltages on single components.

AC circuit –RLC in paralel

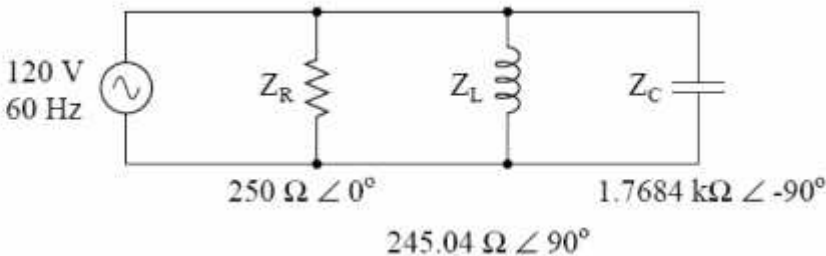
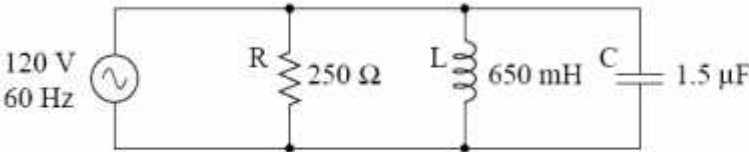


Figure 5.5: Example R, L, and C parallel circuit.

	R	L	C	Total	
E				120 + j0 120 ∠ 0°	Volts
I					Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°		Ohms

	R	L	C	Total	
E	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	Volts
I					Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°		Ohms

Rule of parallel circuits:
 $E_{total} = E_R = E_L = E_C$

AC circuit –RLC in paralel

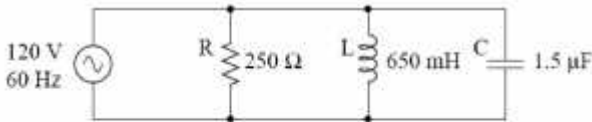


Figure 5.5: Example R, L, and C in parallel

	R	L	C	Total	
E	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	Volts
I	480m + j0 480m ∠ 0°	0 - j489.71m 489.71m ∠ -90°	0 + j67.858m 67.858m ∠ 90°		Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°		Ohms


↑
Ohm's Law
 $I = \frac{E}{Z}$

↑
Ohm's Law
 $I = \frac{E}{Z}$

↑
Ohm's Law
 $I = \frac{E}{Z}$

	R	L	C	Total	
E	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	120 + j0 120 ∠ 0°	Volts
I	480m + j0 480 ∠ 0°	0 - j489.71m 489.71m ∠ -90°	0 + j67.858m 67.858m ∠ 90°	480m - j421.85m 639.03m ∠ -41.311°	Amps
Z	250 + j0 250 ∠ 0°	0 + j245.04 245.04 ∠ 90°	0 - j1.7684k 1.7684k ∠ -90°	141.05 + j123.96 187.79 ∠ 41.311°	Ohms

AC circuit –Complex Circuit

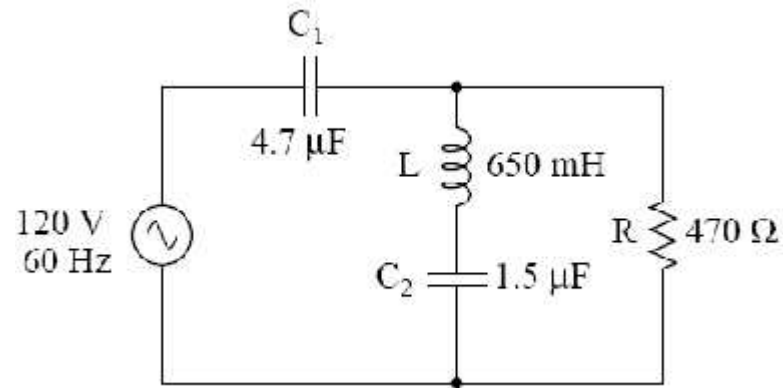

Reactances and Resistances:

$X_{C1} = \frac{1}{2\pi f C_1}$ $X_{C1} = \frac{1}{(2)(\pi)(60 \text{ Hz})(4.7 \mu\text{F})}$ $X_{C1} = 564.38 \Omega$	$X_L = 2\pi f L$ $X_L = (2)(\pi)(60 \text{ Hz})(650 \text{ mH})$ $X_L = 245.04 \Omega$
$X_{C2} = \frac{1}{2\pi f C_2}$ $X_{C2} = \frac{1}{(2)(\pi)(60 \text{ Hz})(1.5 \mu\text{F})}$ $X_{C2} = 1.7684 \text{ k}\Omega$	$R = 470 \Omega$


$$Z_{C1} = 0 - j564.38 \Omega \quad \text{or} \quad 564.38 \Omega \angle -90^\circ$$

$$Z_L = 0 + j245.04 \Omega \quad \text{or} \quad 245.04 \Omega \angle 90^\circ$$

$$Z_{C2} = 0 - j1.7684 \text{ k}\Omega \quad \text{or} \quad 1.7684 \text{ k}\Omega \angle -90^\circ$$

$$Z_R = 470 + j0 \Omega \quad \text{or} \quad 470 \Omega \angle 0^\circ$$

AC circuit –Complex Circuit

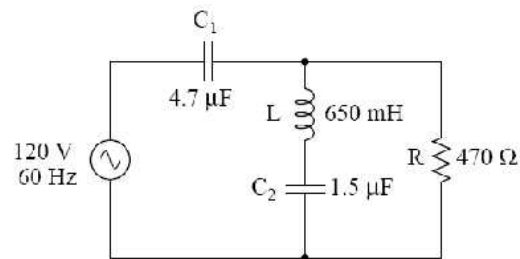

	C_1	L	C_2	R	Total	
E					$120 + j0$ $120 \angle 0^\circ$	Volts
I						Amps
Z	$0 - j564.38$ $564.38 \angle -90^\circ$	$0 + j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684k$ $1.7684k \angle -90^\circ$	$470 + j0$ $470 \angle 0^\circ$		Ohms

The calculation of impedance in this circuit should be completed step by step.

First, serial connection branch of C_2 and L ,

afterwards the parallel branch of resistor and last the serial capacitor effects should be calculated.


	$L - C_2$	$R // (L - C_2)$	$C_1 - [R // (L - C_2)]$	
E			$120 + j0$ $120 \angle 0^\circ$	Volts
I				Amps
Z	$0 - j1.5233k$ $1.5233k \angle -90^\circ$	$429.15 - j132.41$ $449.11 \angle -17.147^\circ$	$429.15 - j696.79$ $818.34 \angle -58.371^\circ$	Ohms

↑
Rule of series
circuits:
 $Z_{L-C_2} = Z_L - Z_{C_2}$

↑
Rule of parallel
circuits:
$$Z_{R/(L-C_2)} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_{L-C_2}}}$$

↑
Rule of series
circuits:
 $Z_{total} = Z_{C_1} + Z_{R/(L-C_2)}$

AC circuit –Complex Circuit

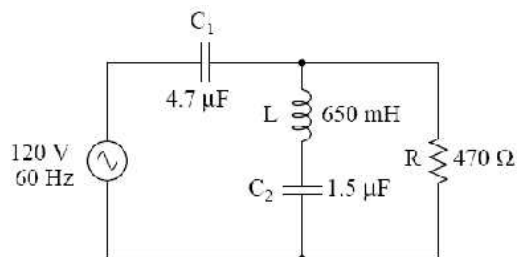

Calculate current drawn from source and passing through C_1

	$L \rightarrow C_2$	$R \parallel (L \rightarrow C_2)$	<i>Total</i> $C_1 \rightarrow [R \parallel (L \rightarrow C_2)]$	
E			$120 + j0$ $120 \angle 0^\circ$	Volts
I			$76.899\text{mA} + j124.86\text{mA}$ $146.64\text{mA} \angle 58.371^\circ$	Amps
Z	$0 - j1.5233\text{k}$ $1.5233\text{k} \angle -90^\circ$	$429.15 - j132.41$ $449.11 \angle -17.147^\circ$	$429.15 - j696.79$ $818.34 \angle -58.371^\circ$	Ohms


↑
Ohm's
Law
 $I = \frac{E}{Z}$

Same current is passing through L - C_2 branch

	$L \rightarrow C_2$	$R \parallel (L \rightarrow C_2)$	<i>Total</i> $C_1 \rightarrow [R \parallel (L \rightarrow C_2)]$	
E			$120 + j0$ $120 \angle 0^\circ$	Volts
I		$76.899\text{mA} + j124.86\text{mA}$ $146.64\text{mA} \angle 58.371^\circ$	$76.899\text{mA} + j124.86\text{mA}$ $146.64\text{mA} \angle 58.371^\circ$	Amps
Z	$0 - j1.5233\text{k}$ $1.5233\text{k} \angle -90^\circ$	$429.15 - j132.41$ $449.11 \angle -17.147^\circ$	$429.15 - j696.79$ $818.34 \angle -58.371^\circ$	Ohms

Rule of series
circuits:
 $I_{\text{total}} = I_{C1} = I_{R/(L \rightarrow C2)}$

AC circuit –Complex Circuit

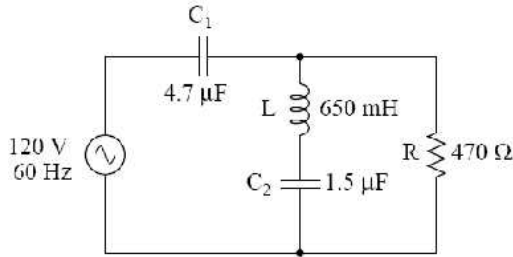

Voltage drop on L-C₂ branch

	$L - C_2$	$R // (L - C_2)$	$C_1 - [R // (L - C_2)]$	
E		$49.533 + j43.400$	$120 + j0$	Volts
		$65.857 \angle 41.225^\circ$	$120 \angle 0^\circ$	
I		$76.899\text{m} + j124.86\text{m}$	$76.899\text{m} + j124.86\text{m}$	Amps
		$146.64\text{m} \angle 58.371^\circ$	$146.64\text{m} \angle 58.371^\circ$	
Z	$0 - j1.5233\text{k}$	$429.15 - j132.41$	$429.15 - j696.79$	Ohms
	$1.5233\text{k} \angle -90^\circ$	$449.11 \angle -17.147^\circ$	$818.34 \angle -58.371^\circ$	


↑
Ohm's
Law
 $E = IZ$

Same Voltage drops on parallel R branch

	$L - C_2$	$R // (L - C_2)$	$C_1 - [R // (L - C_2)]$	
E	$49.533 + j43.400$	$49.533 + j43.400$	$120 + j0$	Volts
	$65.857 \angle 41.225^\circ$	$65.857 \angle 41.225^\circ$	$120 \angle 0^\circ$	
I		$76.899\text{m} + j124.86\text{m}$	$76.899\text{m} + j124.86\text{m}$	Amps
		$146.64\text{m} \angle 58.371^\circ$	$146.64\text{m} \angle 58.371^\circ$	
Z	$0 - j1.5233\text{k}$	$429.15 - j132.41$	$429.15 - j696.79$	Ohms
	$1.5233\text{k} \angle -90^\circ$	$449.11 \angle -17.147^\circ$	$818.34 \angle -58.371^\circ$	

Rule of parallel
circuits:
 $E_{R//(L-C_2)} = E_R = E_{L-C_2}$

AC circuit –Complex Circuit

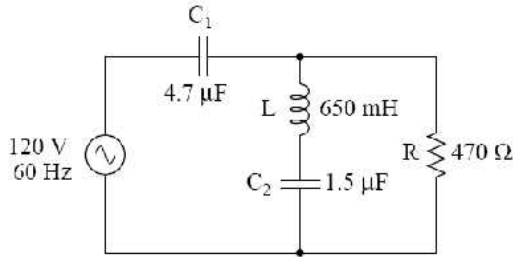

	$L \text{ -- } C_2$	$R \parallel (L \text{ -- } C_2)$	$C_1 \text{ -- } [R \parallel (L \text{ -- } C_2)]$	
E	$49.533 + j43.400$	$49.533 + j43.400$	$120 + j0$	Volts
	$65.857 \angle 41.225^\circ$	$65.857 \angle 41.225^\circ$	$120 \angle 0^\circ$	
I	$-28.490\text{m} + j32.516\text{m}$	$76.899\text{m} + j124.86\text{m}$	$76.899\text{m} + j124.86\text{m}$	Amps
	$43.232\text{m} \angle 131.22^\circ$	$146.64\text{m} \angle 58.371^\circ$	$146.64\text{m} \angle 58.371^\circ$	
Z	$0 - j1.5233\text{k}$	$429.15 - j132.41$	$429.15 - j696.79$	Ohms
	$1.5233\text{k} \angle -90^\circ$	$449.11 \angle -17.147^\circ$	$818.34 \angle -58.371^\circ$	

Ohm's Law

$$I = \frac{E}{Z}$$

	C_1	L	C_2	R	Total	
E					$120 \angle 0^\circ$	Volts
I						Amps
Z	$0 - j564.38$ $564.38 \angle -90^\circ$	$0 + j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684\text{k}$ $1.7684\text{k} \angle -90^\circ$	$470 + j0$ $470 \angle 0^\circ$		Ohms

	C_1	L	C_2	R	
E	$70.467 - j43.400$	$-7.968 - j6.981$	$57.501 + j50.382$	$49.533 + j43.400$	Volts
	$82.760 \angle -31.629^\circ$	$10.594 \angle 221.22^\circ$	$76.451 \angle 41.225^\circ$	$65.857 \angle 41.225^\circ$	
I	$76.899\text{m} + j124.86\text{m}$	$-28.490\text{m} + j32.516\text{m}$	$-28.490\text{m} + j32.516\text{m}$	$105.39\text{m} + j92.341\text{m}$	Amps
	$146.64\text{m} \angle 58.371^\circ$	$43.232\text{m} \angle 131.22^\circ$	$43.232\text{m} \angle 131.22^\circ$	$140.12\text{m} \angle 41.225^\circ$	
Z	$0 - j564.38$	$0 + j245.04$	$0 - j1.7684\text{k}$	$470 + j0$	Ohms
	$564.38 \angle -90^\circ$	$245.04 \angle 90^\circ$	$1.7684\text{k} \angle -90^\circ$	$470 \angle 0^\circ$	

Ohm's Law

$$E = IZ$$

Ohm's Law

$$E = IZ$$

Power in AC circuit



Since it was mentioned, there is a phase shift between current and voltage in AC circuits. The reason is the complex number impedance as it was stated.

So there are three definitions in AC circuits which are related with power.

These are:

- True power (active power),
- Reactive power,
- Apparent power.

Impedance Calculations:

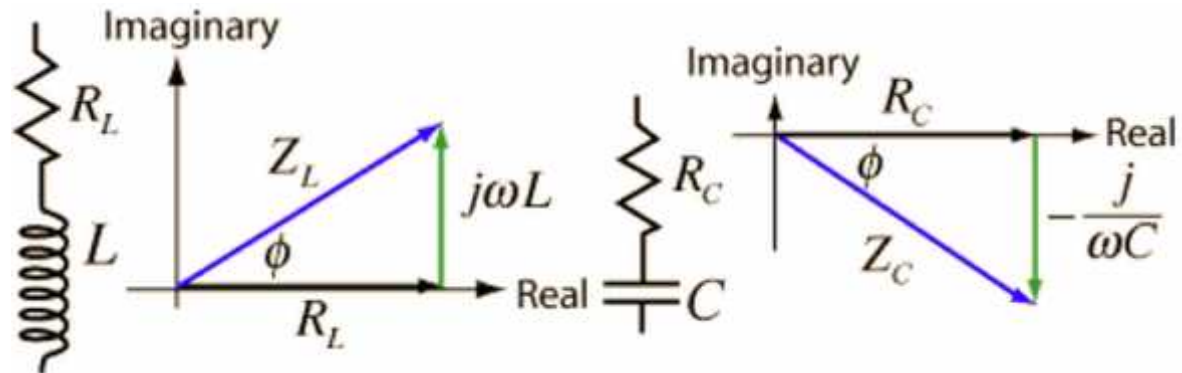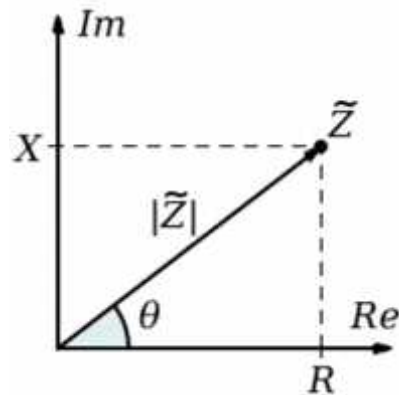

Inductive Circuit

Capacitive Circuit

Power in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


*Measured in units of **Watts***

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

*Measured in units of **Volt-Amps-Reactive (VAR)***

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

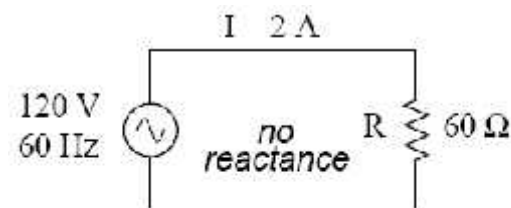
*Measured in units of **Volt-Amps (VA)***



$$P = \text{true power} = I^2 R = 240 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 0 \text{ VAR}$$
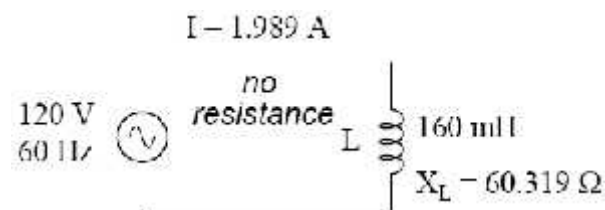
$$S = \text{apparent power} = I^2 Z = 240 \text{ VA}$$



$$P = \text{true power} = I^2 R = 0 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 238.73 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 238.73 \text{ VA}$$

Power in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$

*Measured in units of **Watts***


$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

*Measured in units of **Volt-Amps-Reactive (VAR)***

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

*Measured in units of **Volt-Amps (VA)***

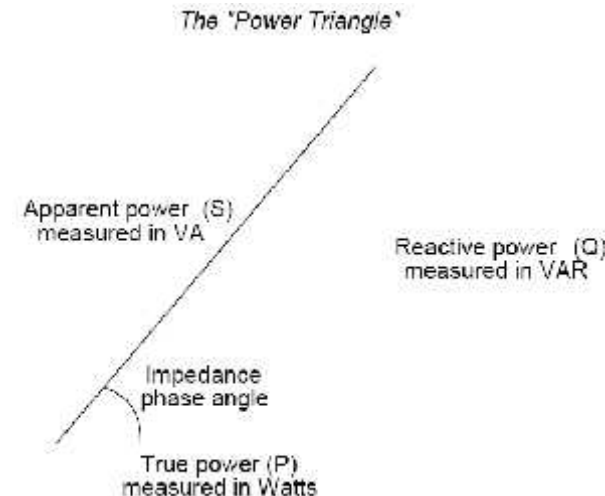The power quantities are scalar quantities. if we consider the 90 degrees of direction angle between the resistor and the reactance and phase shift in the circuit. **This perpendicular triangle is called as 'Power Triangle'**



A part of the power cannot be converted to electrical work in an AC circuit.

The generated effective power is just as the true power.

Power factor is the cosine of the angle between the true and apparent powers ($\cos \phi$).

This value is equal to 1 in only circuits those have just resistors. But if there is a reactance, then the value is between 0 and 1.

Power in AC circuit

$$P - \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of **Watts**

$$Q - \text{reactive power} \quad Q = I^2 X \quad Q = \frac{I^2}{X}$$

Measured in units of **Volt-Amps-Reactive (VAR)**

$$S - \text{apparent power} \quad S = I^2 Z \quad S = \frac{I^2}{Z} \quad S = IE$$

Measured in units of **Volt-Amps (VA)**

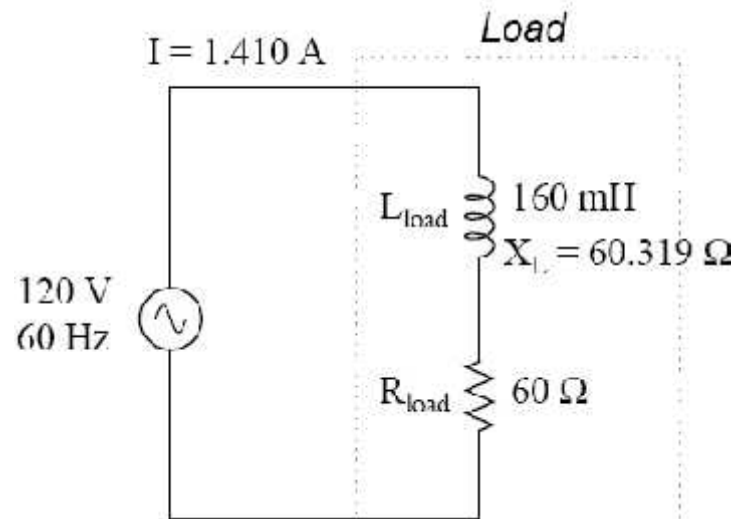

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

$$P - \text{true power} - I^2 R - 119.365 \text{ W}$$

$$Q - \text{reactive power} - I^2 X - 119.998 \text{ VAR}$$

$$S - \text{apparent power} - I^2 Z - 169.256 \text{ VA}$$

The power factor value shows that the **70.5 %** of the power used from the grid is served for the purpose.

Compensation in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{I^2}{R}$$


Measured in units of Watts

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{I^2}{X}$$

Measured in units of Volt-Amps-Reactive (VAR)

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{I^2}{Z} \quad S = IE$$

Measured in units of Volt-Amps (VA)

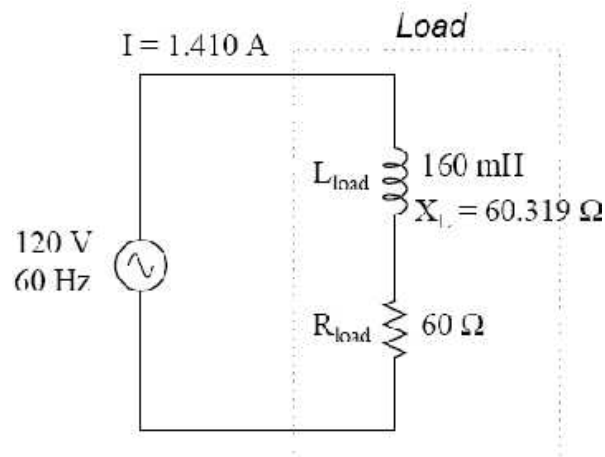

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

The power factor value shows that the **70.5 % of the power used from the grid is served for the purpose.**

This situation is not wanted.

So, in circuit design stage, it must be noted that the power factor is approximately equal to 1.

For this reason, the capacitive and inductive reactance values should be approximately equal to each other.

If this is not possible, a capacitor or an inductor should be externally added to the circuit. **This improvement is called as compensation.**

Compensation in AC circuit

$$P - \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of **Watts**

$$Q - \text{reactive power} \quad Q = I^2 X \quad Q = \frac{I^2}{X}$$

Measured in units of **Volt-Amps-Reactive (VAR)**

$$S - \text{apparent power} \quad S = I^2 Z \quad S = \frac{I^2}{Z} \quad S = IE$$

Measured in units of **Volt-Amps (VA)**

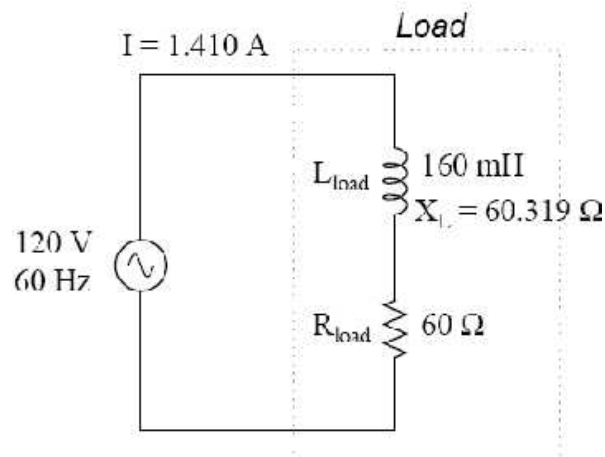

$$P - \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q - \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S - \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

The circuit is inductive so a **parallel** capacitor should be added so that the total reactance of the circuit becomes approximately zero

$$Q = \frac{E^2}{X}$$

... solving for X ...

$$X = \frac{E^2}{Q}$$

$$X = \frac{(120 \text{ V})^2}{119.998 \text{ VAR}}$$

$$X = 120.002 \Omega$$

In parallel branches voltage is constant so the necessary reactance value can be calculated using voltage based power formula

Compensation in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{I^2}{R}$$


Measured in units of Watts

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{I^2}{X}$$

Measured in units of Volt-Amps-Reactive (VAR)

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{I^2}{Z} \quad S = IE$$

Measured in units of Volt-Amps (VA)

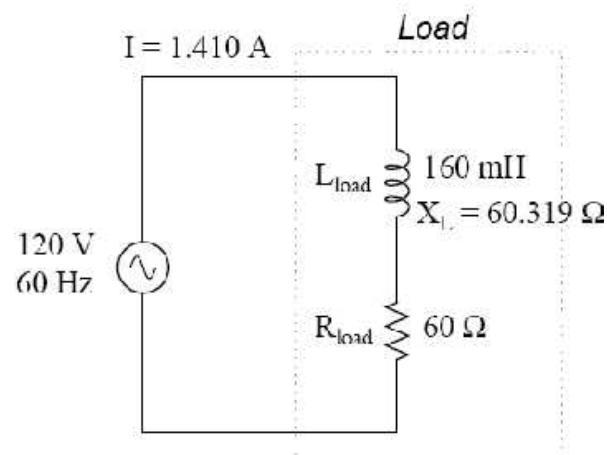

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

The calculated reactance value is used to find capacitor value

$$X_C = \frac{1}{2\pi f C}$$

... solving for C ...

$$C = \frac{1}{2\pi f X_C}$$

$$C = \frac{1}{2\pi(60 \text{ Hz})(120.002 \Omega)}$$

$$C = 22.105 \mu\text{F}$$

Compensation in AC circuit

$$P - \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


*Measured in units of **Watts***

$$Q - \text{reactive power} \quad Q = I^2 X \quad Q = \frac{I^2}{X}$$

*Measured in units of **Volt-Amps-Reactive (VAR)***

$$S - \text{apparent power} \quad S = I^2 Z \quad S = \frac{I^2}{Z} \quad S = IE$$

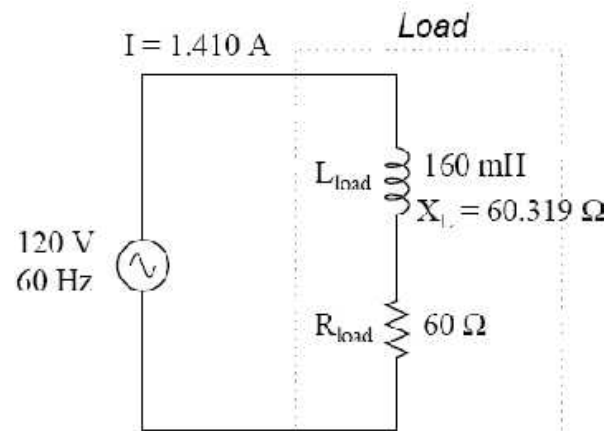*Measured in units of **Volt-Amps (VA)***



$$P - \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q - \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$


$$S - \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

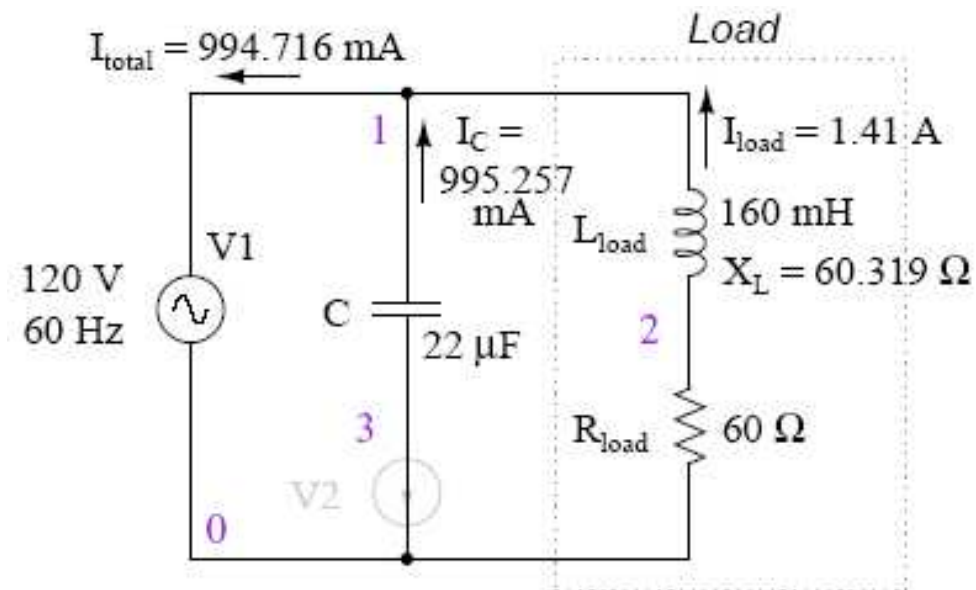The capacitor value found is not a standard value for capacitors, so the closest standard value should be chosen ($22 \mu\text{F}$) and connected in parallel with the circuit.



Compensation in AC circuit

$$P - \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of **Watts**

$$Q - \text{reactive power} \quad Q = I^2 X \quad Q = \frac{I^2}{X}$$

Measured in units of **Volt-Amps-Reactive (VAR)**

$$S - \text{apparent power} \quad S = I^2 Z \quad S = \frac{I^2}{Z} \quad S = IE$$

Measured in units of **Volt-Amps (VA)**

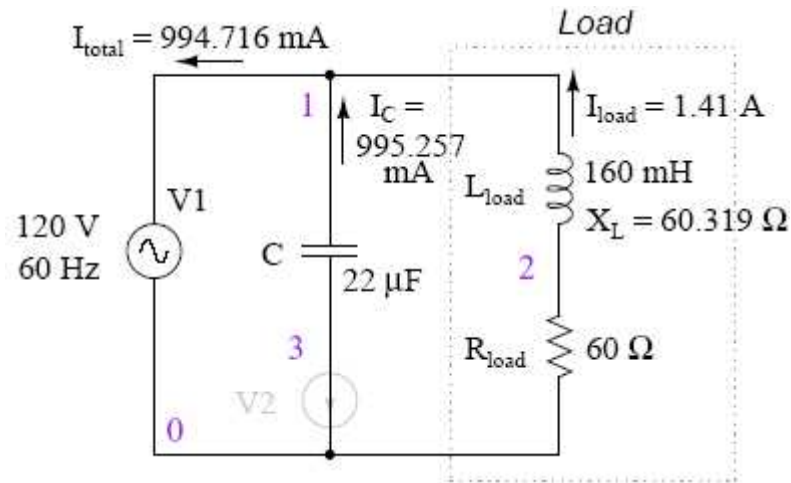

$$Z_{\text{total}} = Z_C \parallel (Z_L \text{ -- } Z_R)$$

$$Z_{\text{total}} = (120.57 \Omega \angle -90^\circ) \parallel (60.319 \Omega \angle 90^\circ \text{ -- } 60 \Omega \angle 0^\circ)$$

$$Z_{\text{total}} = 120.64 - j573.58 \text{ m} \Omega \quad \text{or} \quad 120.64 \Omega \angle 0.2724^\circ$$

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$S = \text{apparent power} = I^2 Z = 119.366 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{119.366 \text{ VA}}$$

$$\text{Power factor} = 0.9999887$$

this improvement made the power factor closer to 1. Besides, the current is decreased.

Compensation in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{I^2}{R}$$


Measured in units of **Watts**

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{I^2}{X}$$

Measured in units of **Volt-Amps-Reactive (VAR)**

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{I^2}{Z} \quad S = IE$$

Measured in units of **Volt-Amps (VA)**

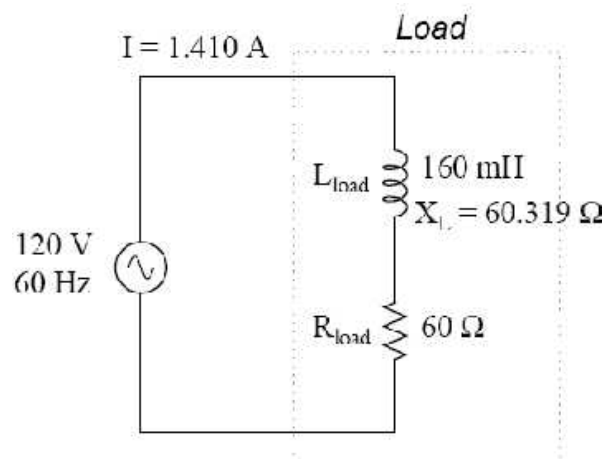

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$


$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True Power}}{\text{Apparent power}} \quad P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}} \quad S = \text{apparent power} = I^2 Z = 169.366 \text{ VA}$$

$$\text{Power factor} = 0.705$$

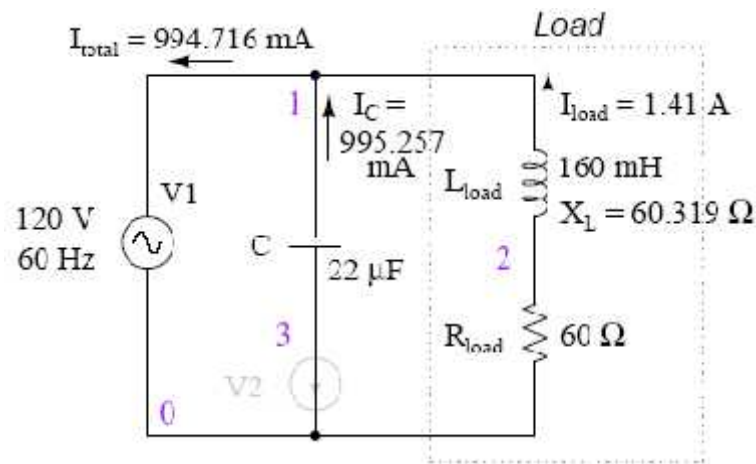

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{119.366 \text{ VA}}$$

$$\text{Power factor} = 0.9999887$$